

APPLICATION NOTE

Gain Block Bias Networks

Introduction

Skyworks gain block amplifiers are InGaP/GaAs HBT integrated circuits. They use a Darlington-pair transistor configuration with bias and feedback resistors properly selected to determine the gain, input and output impedances and bias parameters. A schematic representation of the amplifier is shown in Figure 1.

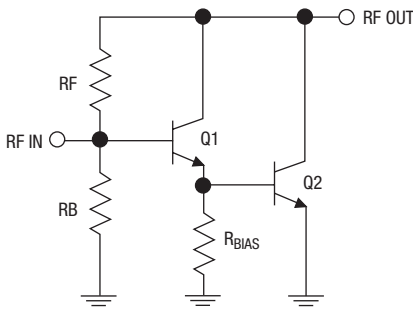


Figure 1. Darlington Pair Amplifier

Abstract

As shown in Figure 2, the amplifier is a two-port device. C1 and C2 provide DC blocking in the RF input and output paths, respectively. RF ground is made through the remaining package pins. The RF output port is also used to provide bias to the amplifier through an external bias network (C4, R1 and L1). The values of the bias decoupling network components are selected based upon the frequency of operation and supply voltage available. This application note provides details on the proper selection of these components.

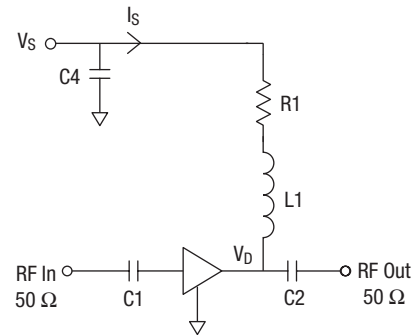


Figure 2. Amplifier with Bias Network

Theory of Operation

Skyworks gain blocks are Darlington feedback amplifiers which feature a constant gain-bandwidth product for use as an RF gain block. They use a circuit topology in which two transistors are combined to form a configuration known as a Darlington pair. This transistor pair behaves like a single transistor with a current gain equivalent to the product of the current gain of the two transistors. Darlington transistors are connected in a common emitter configuration, while sharing the same collector contact.

The emitter current of the first transistor is applied to the base of the second transistor. This gives a high current gain (written β or H_{fe}), and takes less space than two discrete transistors in the same configuration. As RF gain blocks, Darlington pairs are offered as integrated packaged devices, usable from very low frequency to over 10 GHz. They exhibit good broadband matching into 50 Ω and tight performance distributions.

The designed DC voltage that appears at the RF output of the amplifier, known as V_D , is fixed by the base-emitter voltages of Q1 and Q2, and by the voltage divider formed by RF and RB. The values of resistors RF and RB are selected to establish the necessary feedback to set the input and output impedances of the amplifier, as well as to set the base voltages and currents of the Darlington pair. Consequently, the amplifier is controlled by the current supplied to the output node. Thus, the amplifier is biased using a fixed current source rather than a fixed voltage source. The simplest current source is a resistor (R1) connected to a voltage source (V_S) as shown in Figure 2.

APPLICATION NOTE • GAIN BLOCK BIAS NETWORKS

Figure 3 shows a simplified DC equivalent circuit of the Darlington pair gain block. The voltage that appears at the point labeled V_D , which is the RF output of the amplifier, is the series sum of the forward voltages of the base-emitter junctions of the transistors and the voltage drop across RF. The forward voltage of each of the base-emitter diodes is exponentially related to the current flowing through them, and is also affected by temperature.

Since the current through each of the base-emitter diodes directly controls the collector current for each of these transistors (these paths are not shown in this diagram), it is clearly important to control the bias current through each of the base-emitter junctions with a well-regulated current source. If a regulated voltage source is connected to the V_D point in place of current source, the current through the transistors in the amplifier can vary widely in response to comparatively small changes in supply voltage. Additionally, due to the I-V characteristics of the base-emitter junction of each transistor, a small change in voltage or temperature can result in a large change in current.

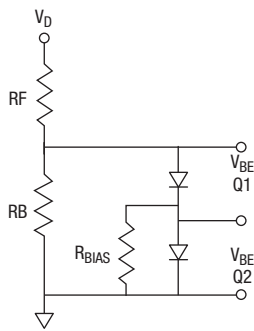


Figure 3. Simplified DC Equivalent Circuit of Darlington Pair Gain Block

Skyworks offers a series of gain block amplifiers in 3 different package styles (see Figure 4). These products differ by such parameters as gain, output power, frequency range and supply current draw, among others. Proper selection of a gain block depends upon the specific requirements of the application. Table 1 shows a list of gain blocks currently offered.

NOTE: For purposes of this application note, the SKY65015-92LF will be referenced. The information provided is common to other Skyworks gain block part numbers. Refer to the data sheets for specific part information.

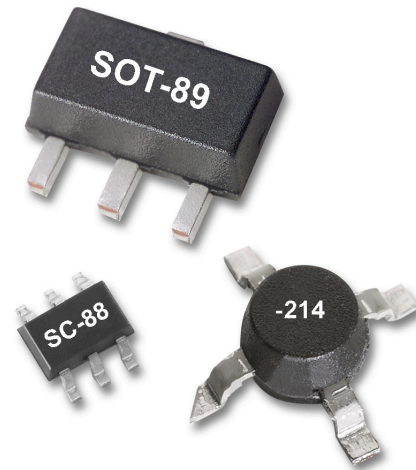


Figure 4. Gain Block Package Styles

Table 1. Skyworks Gain Block Part List

Part Number	Package	Frequency Range (GHz)	Test Frequency (GHz)	Gain Typ. (dB)	Quiescent Current Typ. (mA)	V _{CC} (V)	Noise Figure Typ. (dB)	OIP3 (dBm)	P ₁ dB (dBm)
SKY65013-70LF	SOT-89	LF-7	2	12.5	40	5	5.5	29	12.5
SKY65014-70LF	SOT-89	LF-6	2	16	70	5	4.8	36	18
SKY65015-70LF	SOT-89	LF-6	2	18	70	5	4.2	35	17
SKY65016-70LF	SOT-89	LF-3	2	20	40	5	4.8	27	14
SKY65017-70LF	SOT-89	LF-6	2	20	100	5	4.5	35	20
SKY65013-92LF	SC-88	LF-12	2	12.5	40	5	5.8	29	12.5
SKY65014-92LF	SC-88	LF-9	2	15	70	5	5.4	36	15
SKY65015-92LF	SC-88	LF-6	2	18	70	5	4.8	35	18
SKY65016-92LF	SC-88	LF-3	2	20	40	5	5.4	27	20
SKY65013-214LF	Micro-X	LF-6	2	11.5	40	5	5.4	29	11.5
SKY65014-214LF	Micro-X	LF-6	2	13.5	70	5	4.6	36	13.5
SKY65015-214LF	Micro-X	LF-6	2	16	70	5	5.2	24	16
SKY65016-214LF	Micro-X	LF-3	2	19	40	5	6.5	20	19

The bill of materials for operation at 2 GHz for the SKY65015-92LF gain block amplifier circuit as shown in Figure 2 is shown in Table 2. Capacitors C1 and C2 are selected to provide DC blocking for the RF input and output. Capacitor C4 is used for a bias decoupling capacitor. This capacitor provides suppression of low frequency RF signals appearing across the DC bias lines.

The selection of inductor, L1 is based upon its self-resonant frequency (SRF) and its impedance in the band of operation (F_0). The inductor's SRF should be greater than F_0 and its impedance value should be approximately 10 times greater than Z_0 (50 Ω). Table 3 shows values for inductor L1 based upon the frequency of operation.

Table 2. SKY65015-92LF Bill of Materials

Part	ID	Description	Qty.	Size	Value	Units	Product Number	Manufacturer
1	C1, C2, C4	Capacitor	3	0603	47	nF	GRM188R71E473K	Murata
2	L1	Inductor	1	0603	33	nH	0603CS-33NX_LU	CoilCraft
3	R1	Resistor	1	0603		Ω	See Current Limiting Res. Table	

Table 3. Recommended Chokes by Application Band

Frequency ⁽¹⁾ (GHz)	Inductance (nH)	SRF ⁽²⁾ (GHz)	Impedance (X_L) ⁽³⁾	Mfg. Part Number	Manufacturer
0.4	220	0.82	553	0805CS-221X_L_	CoilCraft
0.8	120	1.10	603	0805CS-121X_L_	CoilCraft
0.9	110	1.10	622	0805CS-111X_L_	CoilCraft
1.2	91	1.33	686	0805CS-910X_L_	CoilCraft
1.6	47	1.70	472	0805CS-470X_L_	CoilCraft
1.8	56	1.90	633	0603CS-56NX_L_	CoilCraft
1.9	47	2.00	561	0603CS-47NX_L_	CoilCraft
2.1	39	2.20	514	0603CS-39NX_L_	CoilCraft
2.2	33	2.30	456	0603CS-33NX_L_	CoilCraft
2.4	27	2.80	407	0603CS-27NX_L_	CoilCraft
3	22	4.60	414	LQW18AN22NJ00	Murata
3.6	22	4.60	497	LQW18AN22NJ00	Murata
4.2	22	4.60	580	LQW18AN22NJ00	Murata
4.9	18	5.50	554	LQW18AN18NJ00	Murata
6	15	6.00	565	LQW18AN15NJ00	Murata

1. Evaluation board L1 nominal value = 33 nH (2.2 GHz). At high microwave frequencies, where no lumped element inductors are available, a ¼ wave length line with a stub may be used.

2. Self-resonant frequency

3. Choke selection is based upon $SRF > F_0$ and impedance ($X_L = 2\pi * F * L$) value 10 times greater than Z_0 (50 Ω). For extreme wideband operation 2 chokes may be combined, i.e. (33 nH and 110 nH).

In most electronic systems, the power supply produces a fixed voltage, rather than a fixed current to the devices comprising the system. The selection of R1 is based upon the system supply voltage available and the value of V_D that occurs when the correct supply DC current is present, as well as the power dissipated by the resistor. The resistor value is derived from the following equation: $R = (V_S - V_D) / I_S$. The minimum resistor power dissipation rating is based upon the power dissipated across the resistor

($P_{DISS} = V^2 * R1$). It is recommended to use resistors rated for at least twice the calculated value of P_{DISS} ; otherwise, use parallel or a series split of several resistors that are each easily capable of dissipating their dissipated power levels. For the evaluation circuit as supplied by Skyworks, the default resistor size is '0603' with a power rating of 1000 mW. Check the manufacturer's power rating when using smaller sized resistors.

Table 4. Current Limiting Resistor Values

V_S (V)	R1 Resistance (Ω)	Minimum Resistor Power Dissipation Rating (mW)	Product Number	Manufacturer
4.4	0.5 ⁽¹⁾	–	ERJ-3GEY0R00V	Panasonic
5	8.2	125	ERJ-3GEYJ8R2V	Panasonic
6	24	250	ERJ-3GEYJ240V	Panasonic
7	36	500	ERJ-3GEYJ360V	Panasonic
8	51	500	ERJ-3GEYJ510V	Panasonic
9	68	1000	ERJ-3GEYJ680V	Panasonic
10	82	1000	ERJ-3GEYJ820V	Panasonic
12	110	1000	ERJ-3GEYJ111V	Panasonic

1. At $V_S = 4.4$ V, the series resistance (R1) is the DC resistance of the bias inductors (L1, L2 and L3) and trace lines.

Low Frequency Operation

For operation with signals below 300 MHz, Ferrite Bead (L2) and Inductor (L3) may be added. Figure 5 shows the schematic for low frequency applications below 300 MHz. Resistor R1 must also be added in series with the inductors to limit the power supply current when the power supply provides a constant voltage, as discussed above.

The modified bill of materials for extreme low frequency performance of the SKY65015-92LF is shown in Table 5. Gain (S_{21}) performance using the bill of materials from Table 2 and Table 5 is shown in Figure 6. The ferrite bead and inductor L3 improve the frequency response below 300 MHz and reduce the variation in bias current, at the cost of degraded performance at 1 GHz and the monetary cost of the components themselves.

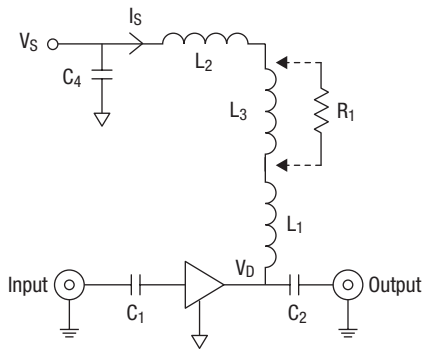


Figure 5. Amplifier with Low Frequency Bias Network

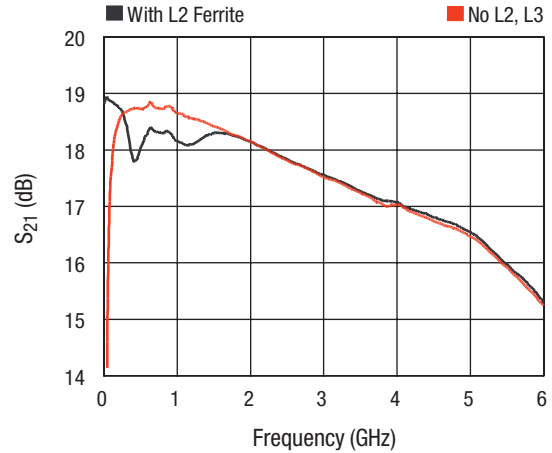


Figure 6. SKY65015-92LF S_{21} vs. Frequency, $I_S = 70$ mA, $T_A = 25$ °C

Table 5. SKY65015-92LF Bill of Materials for Low Frequency Applications

Part	ID	Description	Qty.	Size	Value	Units	Product Number	Manufacturer
1	C1, C2, C4	Capacitor	3	0603	47	nF	GRM188R71E473K	Murata
2	L1	Inductor	1	0603	33	nH	0603CS-33NX_LU	CoilCraft
3	L2	Ferrite Bead	1	1810	1600	Ω	FBMH4525HM162N-T	Taiyo-Yuden
4	L3	Inductor	1	0805	110 nH	nH	0805CS-111X_L_	CoilCraft
5	R1	Resistor	1	0603		Ω	See Current Limiting Res. Table	

Summary

Skyworks gain block amplifiers are InGaP/GaAs HBT integrated circuits using the Darlington-pair transistor configuration which requires a constant DC current applied to the output port to bias the device. Factors such as voltage supply level, system characteristic impedance, frequency of operation and cost should

be taken into account when selecting the proper DC current limiting and RF decoupling bias components and RF DC blocking components in the signal path. The information provided in this application note addresses these tasks. Further information about specific gain block amplifiers may be found in the appropriate data sheets at www.skyworksinc.com.

Copyright © 2008, 2009, Skyworks Solutions, Inc. All Rights Reserved.

Information in this document is provided in connection with Skyworks Solutions, Inc. ("Skyworks") products or services. These materials, including the information contained herein, are provided by Skyworks as a service to its customers and may be used for informational purposes only by the customer. Skyworks assumes no responsibility for errors or omissions in these materials or the information contained herein. Skyworks may change its documentation, products, services, specifications or product descriptions at any time, without notice. Skyworks makes no commitment to update the materials or information and shall have no responsibility whatsoever for conflicts, incompatibilities, or other difficulties arising from any future changes.

No license, whether express, implied, by estoppel or otherwise, is granted to any intellectual property rights by this document. Skyworks assumes no liability for any materials, products or information provided hereunder, including the sale, distribution, reproduction or use of Skyworks products, information or materials, except as may be provided in Skyworks Terms and Conditions of Sale.

THE MATERIALS, PRODUCTS AND INFORMATION ARE PROVIDED "AS IS" WITHOUT WARRANTY OF ANY KIND, WHETHER EXPRESS, IMPLIED, STATUTORY, OR OTHERWISE, INCLUDING FITNESS FOR A PARTICULAR PURPOSE OR USE, MERCHANTABILITY, PERFORMANCE, QUALITY OR NON-INFRINGEMENT OF ANY INTELLECTUAL PROPERTY RIGHT; ALL SUCH WARRANTIES ARE HEREBY EXPRESSLY DISCLAIMED. SKYWORKS DOES NOT WARRANT THE ACCURACY OR COMPLETENESS OF THE INFORMATION, TEXT, GRAPHICS OR OTHER ITEMS CONTAINED WITHIN THESE MATERIALS. SKYWORKS SHALL NOT BE LIABLE FOR ANY DAMAGES, INCLUDING BUT NOT LIMITED TO ANY SPECIAL, INDIRECT, INCIDENTAL, STATUTORY, OR CONSEQUENTIAL DAMAGES, INCLUDING WITHOUT LIMITATION, LOST REVENUES OR LOST PROFITS THAT MAY RESULT FROM THE USE OF THE MATERIALS OR INFORMATION, WHETHER OR NOT THE RECIPIENT OF MATERIALS HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGE.

Skyworks products are not intended for use in medical, lifesaving or life-sustaining applications, or other equipment in which the failure of the Skyworks products could lead to personal injury, death, physical or environmental damage. Skyworks customers using or selling Skyworks products for use in such applications do so at their own risk and agree to fully indemnify Skyworks for any damages resulting from such improper use or sale.

Customers are responsible for their products and applications using Skyworks products, which may deviate from published specifications as a result of design defects, errors, or operation of products outside of published parameters or design specifications. Customers should include design and operating safeguards to minimize these and other risks. Skyworks assumes no liability for applications assistance, customer product design, or damage to any equipment resulting from the use of Skyworks products outside of stated published specifications or parameters.

Skyworks, the Skyworks symbol, and "Breakthrough Simplicity" are trademarks or registered trademarks of Skyworks Solutions, Inc., in the United States and other countries. Third-party brands and names are for identification purposes only, and are the property of their respective owners. Additional information, including relevant terms and conditions, posted at www.skyworksinc.com, are incorporated by reference.