

HIGH-SPEED LEVEL SHIFTING USING Si8XXX ISOLATORS

1. Introduction

Voltage level shifting is common in analog and mixed-signal system applications. While several technologies implement level shifting (e.g., HVIC processes, discrete circuits, dedicated level shifting ICs), recent advances in CMOS isolation technology enables fast, reliable, and highly-integrated ICs that are ideal for a broad range of level shifting applications. This application note discusses precision high-speed level shifting techniques using Skyworks Solutions' Si8xxx Digital isolators and ISOdrivers. Specifically, this application note covers common-mode voltage level shifting, logic threshold voltage level shifting, and gate driver common-mode inversion.

2. Addressing Common Mode Level Shifting

Many industrial applications require measurements of very low-level analog signals from sensors, such as thermocouples and pressure transducers. These sensors often ride on very high common-mode voltages (VCM) and, as a result, have differential outputs. Typically, an instrumentation amplifier applies differential gain to amplify the sensor output signal (typically <100 mV), amplifying the signal to a level compatible with the analog-to-digital converter (ADC) input range (typically >1 V). Since the digitized signal is typically processed by an earth-ground-based MCU or other controller, galvanic isolation is required between the ADC output and ground-based controller input to prevent the high common-mode voltage from entering low-voltage, ground-based circuitry.

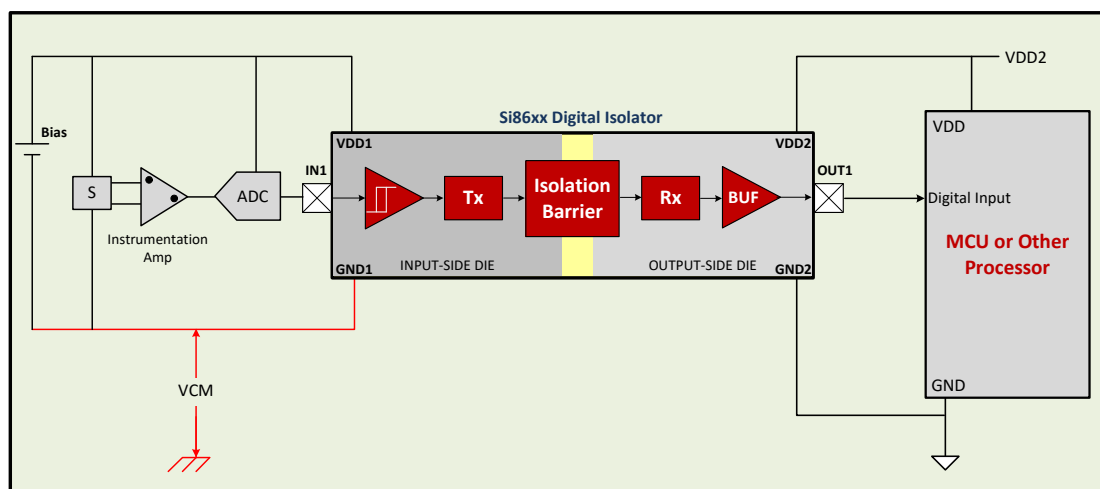


Figure 1. Example Industrial Application

Figure 1 shows a Skyworks Solutions Si86xx digital isolator providing isolation and level-shifting between an analog data acquisition circuit (riding on a high common-mode voltage) and a ground-referenced controller. The Si86xx isolator operates by enabling its input-side transmitter when IN1 is logic high, causing the transmitter to generate a carrier wave that propagates through the isolation barrier to the output-side receiver. The receiver asserts a logic high on OUT1 when sufficient in-band energy is detected. Conversely, a logic low at IN1 results in no carrier, which, in turn, results in a logic low at OUT1. This simple architecture carries with it industry-leading performance, reliability, power savings, integration, cost effectiveness, and space savings. These isolators are very easy to use; the designer need only choose the isolation working voltage rating, speed, and dc bias. (Note the difference between working voltage and rated voltage; rated voltage is a component-level specification that specifies the isolator's voltage withstand capability at 2500 V_{RMS} or 5000 V_{RMS} for one minute.) In Figure 1, the VCM is 560 V (peak or dc) and is also the working voltage for the system, i.e. the voltage that the barrier must withstand continuously throughout the system's lifetime. As shown in Figure 2, the mean time-to-failure for these isolators at a working voltage of 1000 V_{RMS} (1414Vpk) is 100 years.

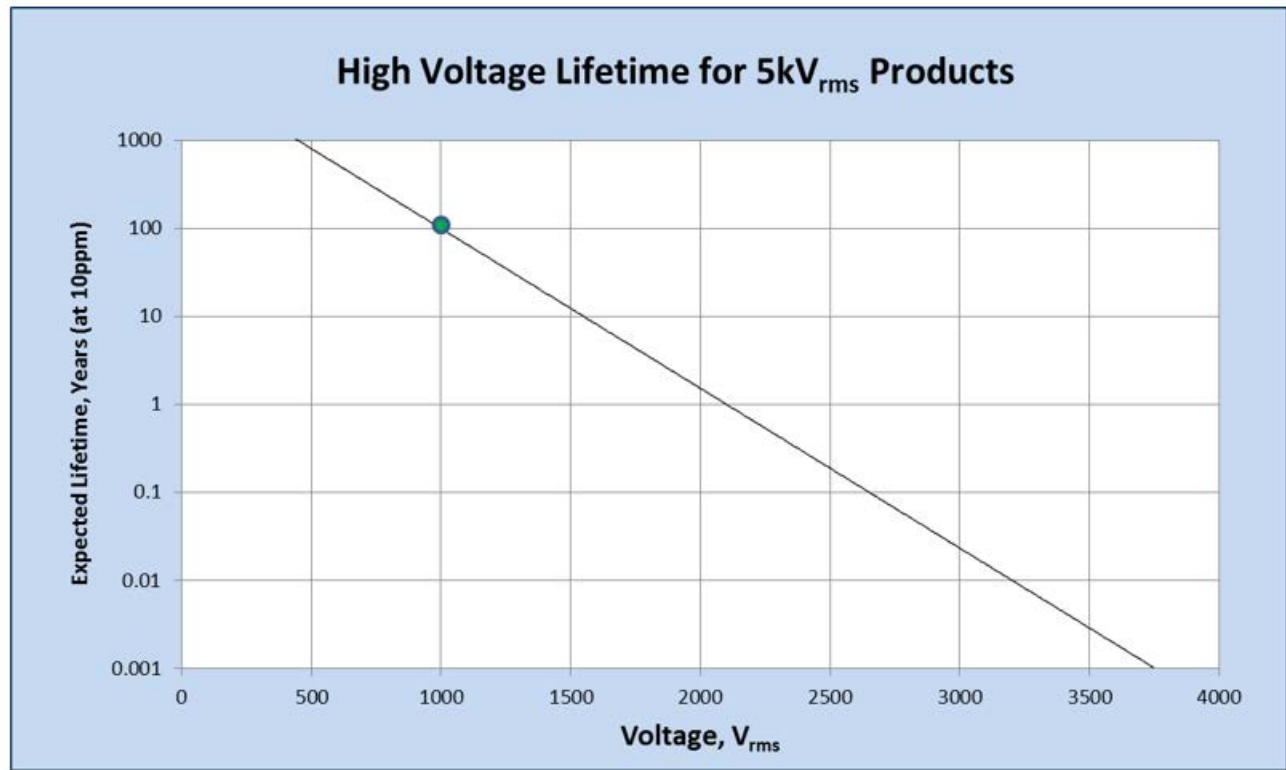


Figure 2. Si86xx Time-Dependent Dielectric Breakdown

3. Logic Level Shifting

To reduce overall system power consumption, many of today's high-speed logic devices (e.g. FPGAs) operate from supplies of 3V or less. Lower bias voltages (and consequently lower logic thresholds) complicate interface with 5 V devices, creating a need for a fast and robust logic level shifter. The “minimalist” approach of Figure 3A provides compatible logic thresholds, but the maximum 4.8 V V_{OH} of the 5 V logic device can negatively impact the performance or damage the 2.5 V logic device. Figure 3B eliminates the over-voltage problem of Figure 3A using an open drain (or open collector) buffer with a pull-up to 2.5 V. While this is a good solution for low-speed logic circuits, the pull-up resistor can significantly slow the rising edge of the output waveform, creating timing problems in high-speed circuits. Figure 3C shows the Si86xx isolator used as a logic threshold level shifter where each side of the isolator is biased to match the local logic rails. Note the common ground on both sides of the isolator since all logic supplies are assumed to be connected to a common ground.

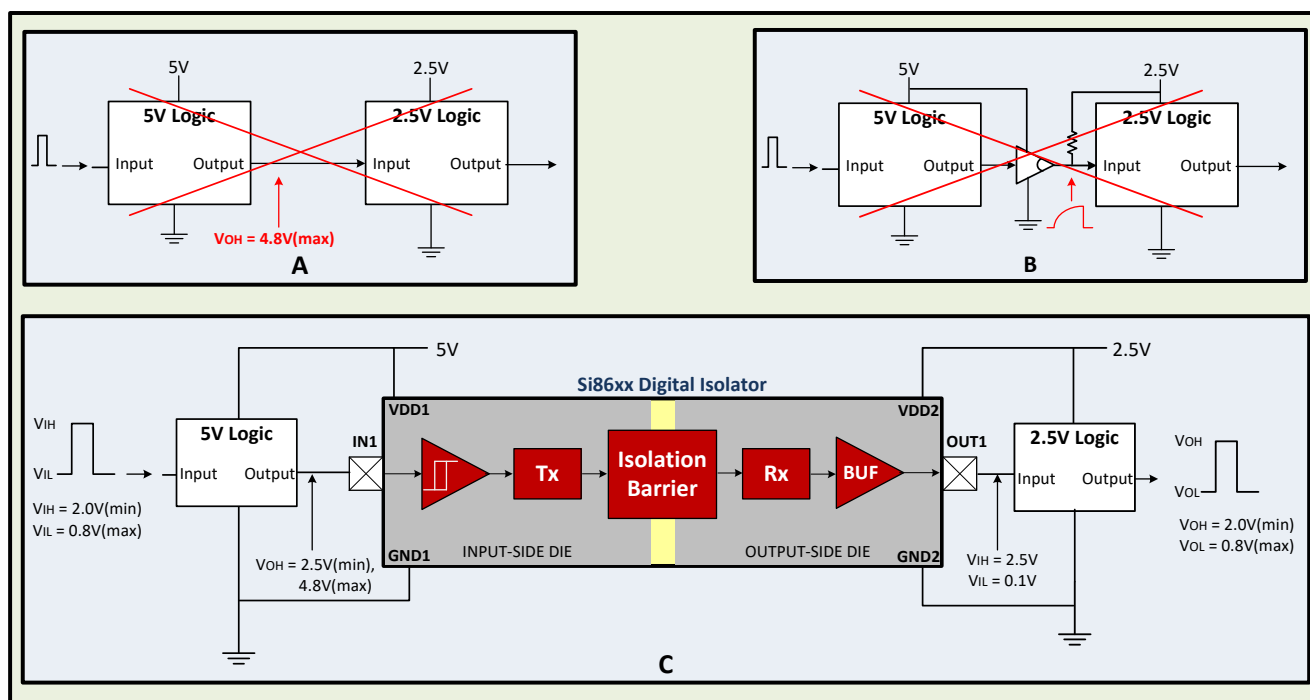


Figure 3. Logic Level Shift Approaches

4. Isolated Gate Driver Common Mode Inversion

The Si823x ISOdrivers are isolated dual 0.5 A and 4.0 A MOSFET/IGBT gate drivers based on the same proprietary Skyworks Solutions CMOS isolation technology used in the Si86xx digital isolators. ISOdrivers provide up to 5 kVRMS withstand voltage per UL1577 and have fast 60 ns propagation delay time. Their high integration, flexibility, and performance allow these drivers to be used in a number of switch mode power system (SMPS) applications. The Dual ISOdrivers have no built-in overlap protection or dead time generator, enabling the state of each driver output to unconditionally follow that of its input as long as both sides of the device are powered. A block diagram of the Si823x Dual ISOdriver is shown in Figure 4.

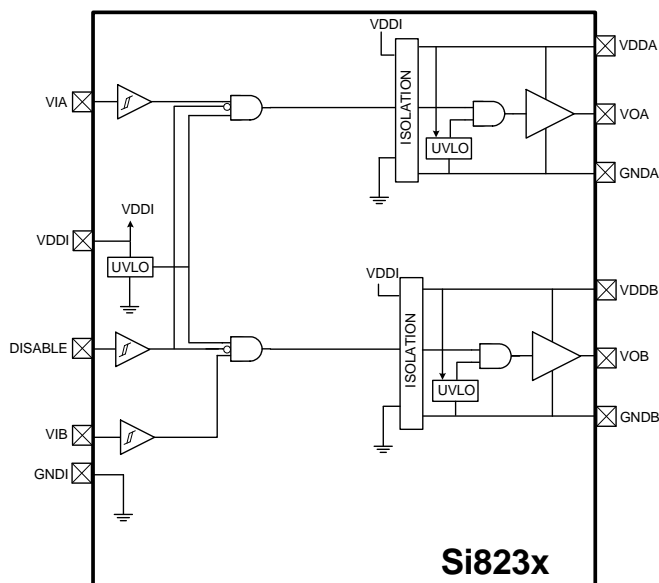


Figure 4. Common Mode Inversion

For example, in a given application, GNDA might have a common-mode voltage of 100 V while GNDB has a common-mode voltage of 200 V. These two common-mode voltages can reverse (i.e., GNDA can change to 200 V, and GNDB can change to 100 V as in Figure 5) without damaging or upsetting the driver. The Si823x drivers can therefore be used in dual-low-side, dual-high-side, or high-side/low-side configurations in systems where common-mode voltages vary greatly.

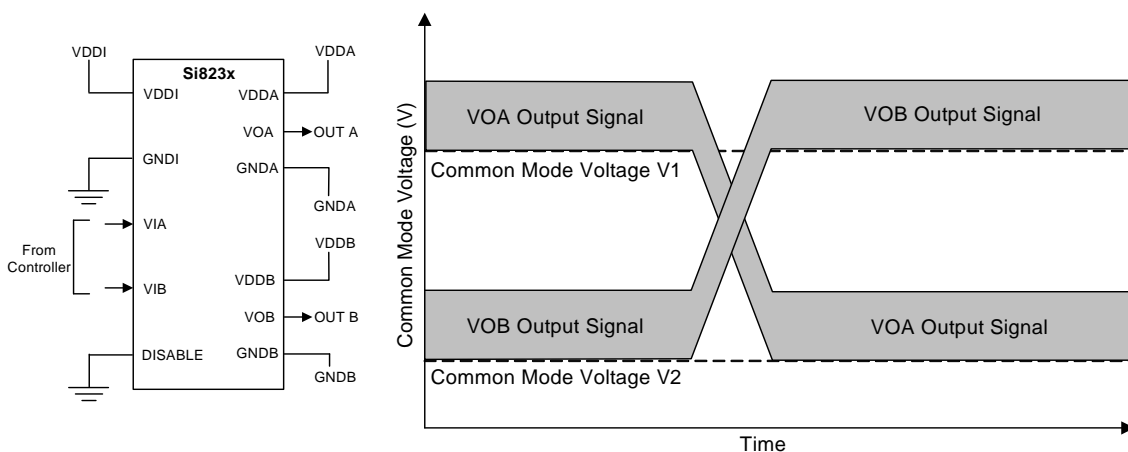


Figure 5. Common Mode Inversion

5. Summary

This application note discusses high-speed level shifting techniques using Skyworks Solutions' Si8xxx digital isolators and ISOdrivers. The underlying technology of Skyworks Solutions CMOS isolation technology offers high-speed and low-power operation, high reliability and integration, and ease-of-use for voltage level-shifting as well as other applications.

DOCUMENT CHANGE LIST

Revision 0.1 to Revision 0.2

- Removed Si84xx
- Changed Si8232/5/6 specific part number to Si823x
- Updated Figure 2 from 2.5 kV_{RMS} to 5 kV_{RMS}




**Connecting Everyone
and Everything,
All the Time**



Portfolio

www.skyworksinc.com

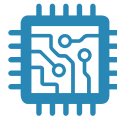

Quality

www.skyworksinc.com/quality



Support & Resources

www.skyworksinc.com/support

Copyright © 2021 Skyworks Solutions, Inc. All Rights Reserved.

Information in this document is provided in connection with Skyworks Solutions, Inc. ("Skyworks") products or services. These materials, including the information contained herein, are provided by Skyworks as a service to its customers and may be used for informational purposes only by the customer. Skyworks assumes no responsibility for errors or omissions in these materials or the information contained herein. Skyworks may change its documentation, products, services, specifications or product descriptions at any time, without notice. Skyworks makes no commitment to update the materials or information and shall have no responsibility whatsoever for conflicts, incompatibilities, or other difficulties arising from any future changes.

No license, whether express, implied, by estoppel or otherwise, is granted to any intellectual property rights by this document. Skyworks assumes no liability for any materials, products or information provided hereunder, including the sale, distribution, reproduction or use of Skyworks products, information or materials, except as may be provided in Skyworks' Terms and Conditions of Sale.

THE MATERIALS, PRODUCTS AND INFORMATION ARE PROVIDED "AS IS" WITHOUT WARRANTY OF ANY KIND, WHETHER EXPRESS, IMPLIED, STATUTORY, OR OTHERWISE, INCLUDING FITNESS FOR A PARTICULAR PURPOSE OR USE, MERCHANTABILITY, PERFORMANCE, QUALITY OR NON-INFRINGEMENT OF ANY INTELLECTUAL PROPERTY RIGHT; ALL SUCH WARRANTIES ARE HEREBY EXPRESSLY DISCLAIMED. SKYWORKS DOES NOT WARRANT THE ACCURACY OR COMPLETENESS OF THE INFORMATION, TEXT, GRAPHICS OR OTHER ITEMS CONTAINED WITHIN THESE MATERIALS. SKYWORKS SHALL NOT BE LIABLE FOR ANY DAMAGES, INCLUDING BUT NOT LIMITED TO ANY SPECIAL, INDIRECT, INCIDENTAL, STATUTORY, OR CONSEQUENTIAL DAMAGES, INCLUDING WITHOUT LIMITATION, LOST REVENUES OR LOST PROFITS THAT MAY RESULT FROM THE USE OF THE MATERIALS OR INFORMATION, WHETHER OR NOT THE RECIPIENT OF MATERIALS HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGE.

Skyworks products are not intended for use in medical, lifesaving or life-sustaining applications, or other equipment in which the failure of the Skyworks products could lead to personal injury, death, physical or environmental damage. Skyworks customers using or selling Skyworks products for use in such applications do so at their own risk and agree to fully indemnify Skyworks for any damages resulting from such improper use or sale.

Customers are responsible for their products and applications using Skyworks products, which may deviate from published specifications as a result of design defects, errors, or operation of products outside of published parameters or design specifications. Customers should include design and operating safeguards to minimize these and other risks. Skyworks assumes no liability for applications assistance, customer product design, or damage to any equipment resulting from the use of Skyworks products outside of Skyworks' published specifications or parameters.

Skyworks, the Skyworks symbol, Sky5®, SkyOne®, SkyBlue™, Skyworks Green™, Clockbuilder®, DSPLL®, ISOModem®, ProSLIC®, and SiPHY® are trademarks or registered trademarks of Skyworks Solutions, Inc. or its subsidiaries in the United States and other countries. Third-party brands and names are for identification purposes only and are the property of their respective owners. Additional information, including relevant terms and conditions, posted at www.skyworksinc.com, are incorporated by reference.

Skyworks Solutions, Inc. | Nasdaq: SWKS | sales@skyworksinc.com | www.skyworksinc.com

USA: 781-376-3000 | Asia: 886-2-2735 0399 | Europe: 33 (0)1 43548540 | [in](#) [f](#) [t](#) [y](#)